GET BETTER AT PHYSICS · MARK SCHEME

Potential Dividers: tiered multiple choice

AQA A-level Physics · 7407 / 7408 · Specification 3.5.1.5 · 4 questions · 4 marks

1 mark per correct letter | Worked reasoning for every question

How students did = from AQA examiner reports, where available

Answer key

Q1	Q2	Q3	Q4
B	C	A	D

Easy

Question 1

1 **B**

A voltmeter that loads the circuit · AQA June 2019 · AS Paper 2 · Q32

The voltmeter (R) is in parallel with Y (R/2): combined resistance = (R × R/2) / (R + R/2) = R/3. This is in series with X (R), so the voltmeter reads 6.0 × (R/3) / (R + R/3) = 6.0 × ¼ = 1.5 V.

> **Watch out:** 2.0 V would be right for an ideal voltmeter. This one has resistance R, which lowers the resistance across Y.

How students did: Over half of students got this right in June 2019.

Medium

Questions 2–4

2 **C**

Range of a potential divider · AQA June 2023 · AS Paper 2 · Q30

The voltmeter is across the 3.0 kΩ resistor and the variable resistor. V = 9.0 × (3.0 + x) / (6.0 + x), with x in kΩ. At x = 0: 9.0 × 3.0 / 6.0 = 4.5 V. At x = 3.0 kΩ: 9.0 × 6.0 / 9.0 = 6.0 V. So the range is 4.5 V to 6.0 V.

> **Watch out:** The variable resistor changes the total resistance too, so the voltmeter reading never reaches 0 V or 9.0 V.

3 **A**

Balancing a resistance wire against two resistors · AQA June 2025 · AS Paper 2 · Q7

Zero current means P is at the same potential as the junction of M and N, so XP : PY = M : N. If N's resistance increases, M's share of the pd falls, so the balance point moves towards X. Changing the wire's resistance (B) or the cell (C and D) changes both sides by the same factor, so the balance point would not move.

How students did: In June 2025 the correct answer was the most popular choice.

4 **D**

Temperature-sensing circuit · AQA 2020 · AS Paper 2 · Q34

When the temperature falls, the thermistor's resistance increases. The total resistance rises, so the current (ammeter) decreases. The thermistor now has a bigger share of the total resistance, so the pd across it (voltmeter) increases.

End of mark scheme. Answers from AQA's published keys; explanations written for this pack. AQA material is © AQA. More free packs and 1-to-1 tuition: **www.getbetteratphysics.co.uk**

GET BETTER AT PHYSICS · WHAT NEXT?

Got some of these wrong?

Good. The questions you got wrong show you exactly what to work on next. The quickest way to fix them is to work through them with someone who marks these papers.

Book a free 15-minute call

Tell me which questions caught you out. We'll talk about what's going wrong and whether 1-to-1 or small-group tuition would help. There's no obligation.

Book your free call

calendly.com/getbetteratphysics/freechat

Scan to book

Current AQA examiner
I know what the mark schemes reward and where marks are lost.

Matched to your exam board
Sessions follow your specification and the topics you find hardest.

Pay per session
No block booking. 1-to-1 or small groups of up to 4.

More free packs

Tiered past-paper questions with full mark schemes, sorted by topic.
getbetteratphysics.co.uk/free-revision-packs

Masterclasses are coming

Want to hear first? Email **helpme@getbetteratphysics.co.uk** and I'll let you know when dates are announced.

Parents: I use these packs in my own tutoring sessions. Tuition options and prices:
getbetteratphysics.co.uk/tuitionpricing

Free revision resource · not for resale