GET BETTER AT PHYSICS · MARK SCHEME

Resistance & I–V Characteristics: tiered multiple choice

AQA A-level Physics · 7407 / 7408 · Specification 3.5.1.2 · 4 questions · 4 marks

1 mark per correct letter

Worked reasoning for every question

How students did = from AQA examiner reports, where available

Answer key

Q1	Q2	Q3	Q4
A	B	C	D

Easy

Question 1

1 **A**

Resistor and diode in series · AQA June 2016 · AS Paper 2 · Q29

No current flows until the pd across the diode reaches its threshold (about 0.6 V), so the graph starts along the V axis. After that the resistor limits the current, so the current rises in a roughly straight line: graph A.

How students did: 55% of students got this right in June 2016.

Medium

Questions 2–4

2 **B**

I–V graph of a filament lamp · AQA June 2019 · AS Paper 2 · Q29

As the current increases the filament gets hotter and its resistance increases. Each extra volt then gives a smaller increase in current, so the graph curves towards the voltage axis: graph B.

> **Watch out:** C curves the other way: that would mean the resistance decreases as the lamp heats up.

How students did: The success rate on this question was quite low in June 2019.

3 **C**

Finding the ohmic conductor with least resistance · AQA June 2025 · AS Paper 2 · Q18

An ohmic conductor has a constant V / I. For A: 2.0 / 0.3 = 4.0 / 0.6 = … = 6.7 Ω, constant. For C: 2.0 / 0.6 = 4.0 / 1.2 = … = 3.3 Ω, constant. B and D are not ohmic. C has the smaller resistance.

> **Watch out:** B has the largest currents, but its V / I changes along the table, so it is not ohmic.

How students did: In June 2025 slightly more students chose B than the correct answer.

4 **D**

Two components in parallel · AQA 2021 · AS Paper 2 · Q31

In parallel, each component has the full 12 V across it. Read each graph at 12 V: about 14.0 mA for the straight line and about 9.0 mA for the dashed curve. The battery supplies the sum: 23.0 mA.

> **Watch out:** 7.9 mA (A) is where the two graphs cross. That would only matter if the components were in series and shared the same current.

End of mark scheme. Answers from AQA's published keys; explanations written for this pack. AQA material is © AQA. More free packs and 1-to-1 tuition: **www.getbetteratphysics.co.uk**

GET BETTER AT PHYSICS · WHAT NEXT?

Got some of these wrong?

Good. The questions you got wrong show you exactly what to work on next. The quickest way to fix them is to work through them with someone who marks these papers.

Book a free 15-minute call

Tell me which questions caught you out. We'll talk about what's going wrong and whether 1-to-1 or small-group tuition would help. There's no obligation.

Book your free call

calendly.com/getbetteratphysics/freechat

Scan to book

Current AQA examiner
I know what the mark schemes reward and where marks are lost.

Matched to your exam board
Sessions follow your specification and the topics you find hardest.

Pay per session
No block booking. 1-to-1 or small groups of up to 4.

More free packs

Tiered past-paper questions with full mark schemes, sorted by topic.
getbetteratphysics.co.uk/free-revision-packs

Masterclasses are coming

Want to hear first? Email **helpme@getbetteratphysics.co.uk** and I'll let you know when dates are announced.

Parents: I use these packs in my own tutoring sessions. Tuition options and prices:
getbetteratphysics.co.uk/tuitionpricing

Free revision resource · not for resale